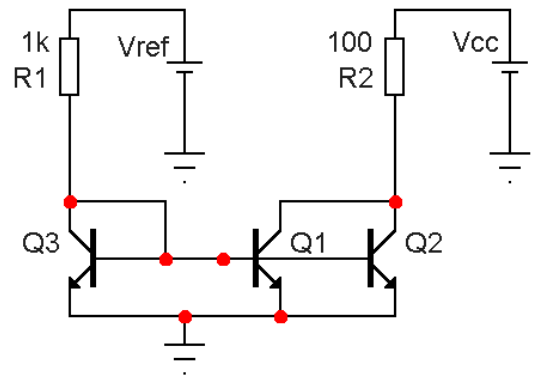


1. $V_{CC}=20$ Volt, $V_{be} = 0.7$ Volt and $\beta=10$

a. Calculate V_{ref} to make $I_{R2}=100\text{mA}$

Bereken V_{ref} zodat $I_{R2}=100\text{mA}$

Answer: $V_{ref}=65.7$ Volt




2. $V_{CC}=20$ Volt, $\beta=10$

a. Calculate V_{ref} to make $I_{R2}=100\text{mA}$

Bereken V_{ref} zodat $I_{R2}=100\text{mA}$

Answer: $V_{ref}=52.76$ Volt

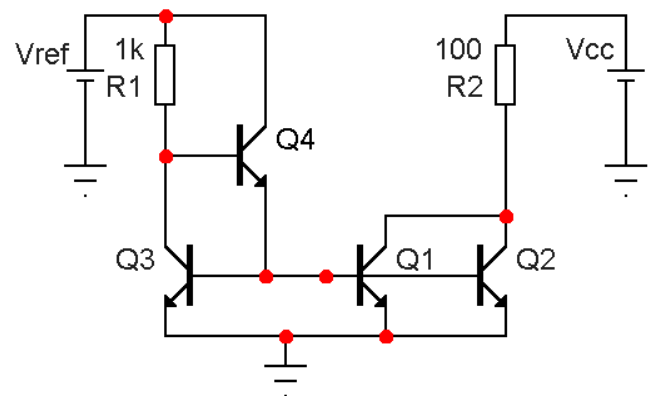

3. $\beta_{1,2,3} = \infty$ $V_{be} = 0.7$ Volt, $V_{ref}=10$ Volt

a. Calculate I_{R1}


Bereken I_{R1} als $V_{ref}=0$ Volt

b. Calculate minimum value for V_{CC} ($V_{cb(Q3)}=0.5$ Vmin.)

Bereken minimale waarde van V_{CC} ($V_{cb(Q3)} = 0.5$ Vmin.)

Answers: $I_{R1}=10.6\text{mA}$

$V_{CC_{min}} = 0.2$ Volt

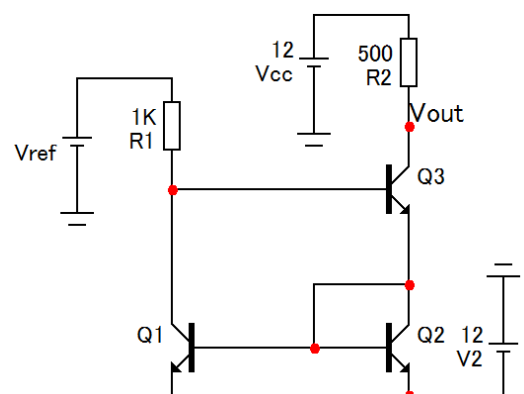

4. $R_1 = 47\Omega$, $R_2 = 10R_1$ and $I_1=10\text{mA}$, $V_{cb(Q1)} > 0.5\text{Volt}$

$\beta_{Q1} = \beta_{Q2}$ Early voltage is infinity and $V_{be(Q1)} = V_{be(Q2)}$

a. Calculate the current through R3


Bereken de stroom door R3

b. Calculate the maximum value for R3

Bereken de maximale waarde voor R3


Answers: $I_{R3} = 1\text{mA}$

$R_3 < 18.33$ K

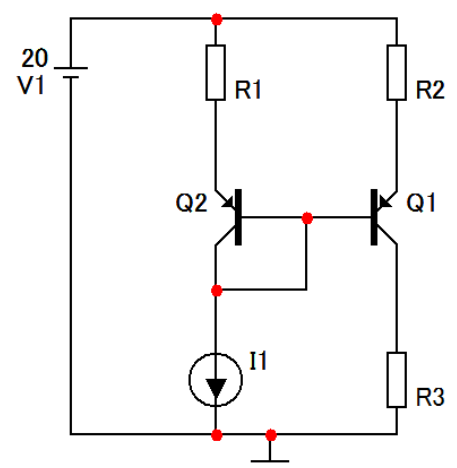

5. $V_{be} = 0.7\text{Volt}$ $\beta_{1,2,3,4,5,6} = \infty$
 $V_G = 0.1 \times \sin(\omega t)$

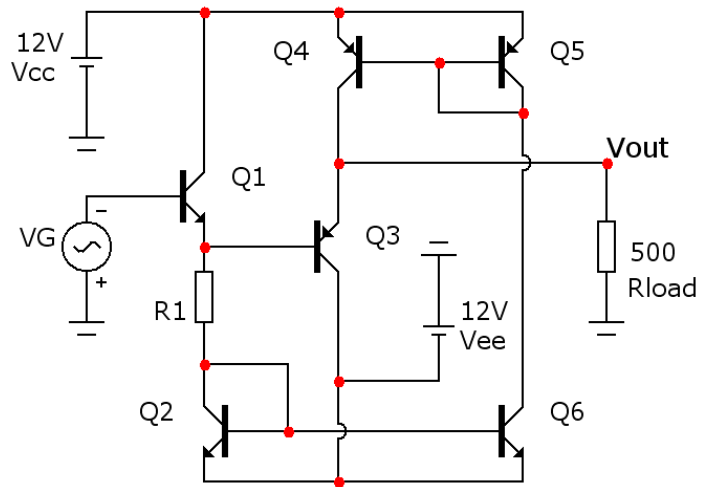- a. Find the DC-value for V_{out} if $I_{c1} = I_{c3}$.
 This should not be calculated. Give a short explanation
- b. Calculate R_1 to make $I_{e1} = 5\text{mA}$
 Answers:
 a. V_{out} is zero, because $I_{e1} = I_{e2}$, results in $V_{be1} = V_{be2}$
 b. $R_1 = 2260$




6. $V_{be(Q1)} = V_{be(Q2)} = 0.7\text{ Volt}$
 $\beta_{Q1, Q2} = 10$

- a. Find the DC current through R_e
- b. Calculate the current through R_2
- c. Calculate the voltage V_{c1}

Answer questions d,e and f with:
 $R_6 = 20\text{K}$ and $R_9 = 30\text{K}$
All betas are infinity !!!!!

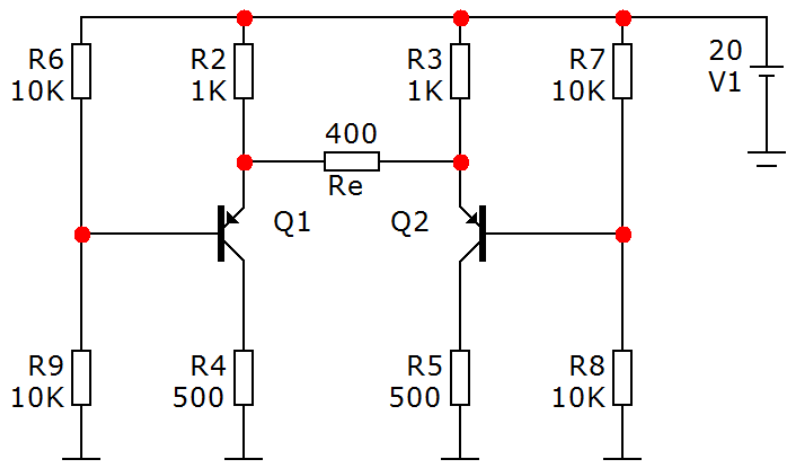- d. Calculate the DC current through R_e
- e. Calculate the current through R_2
- f. Calculate the voltage V_{c1}



- Answers:
- a. Zero because of balanced condition
 - b. $I_{R2} = 6.39\text{ mA}$
 - c. $V_{c1} = 2.9\text{ Volt}$
 - d. $I_{Re} = 5\text{mA}$
 - e. $I_{R2} = 7.3\text{mA}$
 - f. $V_{c1} = 1.15\text{ Volt}$

7. $\beta_{1,2} = \infty$ and $V_{be} = 0.7$ Volt

$$V_{in} = 1mV \sin(2000\pi t)$$

a. Calculate I_{cQ1} and I_{cQ2}

Bereken I_{cQ1} en I_{cQ2}

b. Calculate V_{cQ1} referred to ground

Bereken V_{cQ1} t.o.v. aarde

c. Draw the small signal equivalent circuit


Teken het klein signaal vervangingschema

d. Calculate the signal voltage at the base of Q_1

Bereken de signaalspanning op de basis van Q_1

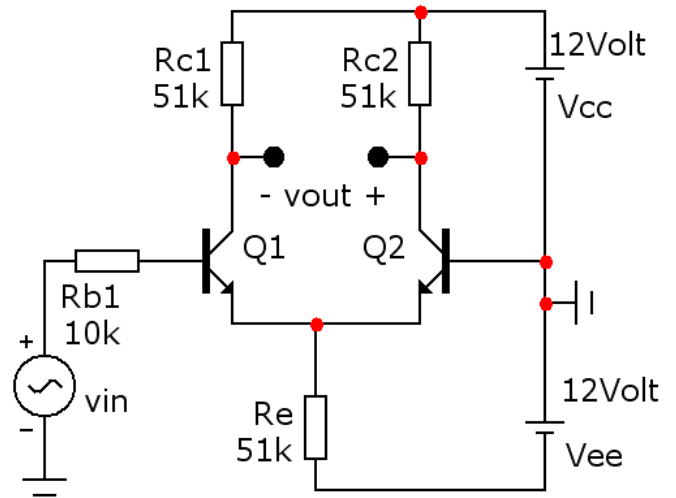e. Use the small equivalent circuit to calculate the gain

$$A_v = \frac{v_{out}}{v_{in}} \text{ Neglect the signal current through } R_e$$



Gebruik het klein signaal vervangingschema ter bepaling van de versterking $A_v = \frac{v_{out}}{v_{in}}$ Verwaarloos

de signaalstroom door R_e

f. Calculate the amplitude of $v_{cQ1}(t)$ referred to ground

Bereken de amplitude of $v_{cQ1}(t)$ t.o.v. aarde

Answers: a. collector currents 0.111mA, b. $V_{c(Q1)} = 6.35$ Volt, c. See textbook, d. $v_{b(Q1)} =$ equal to v_{in}

e. $A_v = 218$, f. $v_{c(Q1)} = 109$ mV


8. Current gain of Q_1, \dots, Q_3 is 75

Output resistance Q_3 is 200 $K\Omega$

a. Calculate the common mode gain (A_{vc})

$$A_{vc} = \frac{v_{c(Q1)}}{V_i} \text{ (definition)}$$

Answer: $A_{vc} = 25e-3$

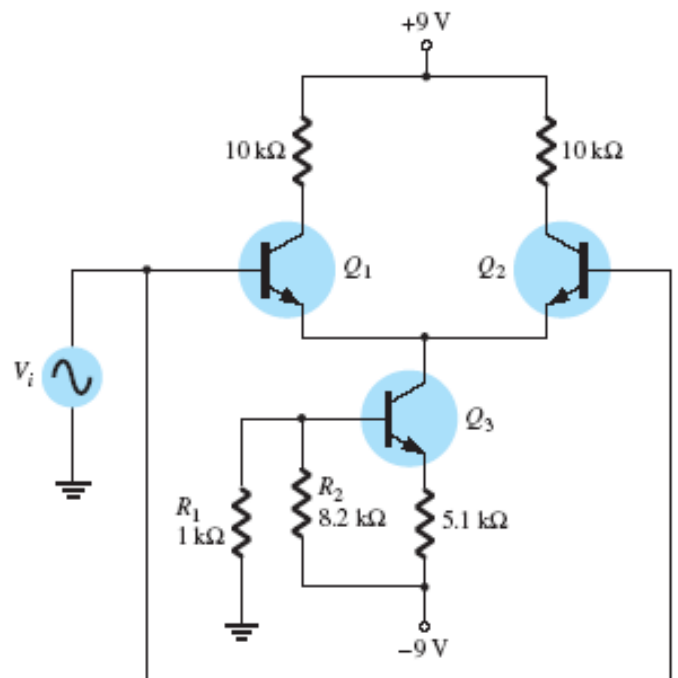


9. $R_1=R_2=200\Omega$
 $\beta_1=\beta_2=\beta=20$
 $\beta_3=\beta_4=\beta_5=\beta_6=\infty$

a. Find the numerical value of the gain

$$A_{v1} = \frac{v_{out1}}{v_b(Q_2)}$$

b. $A_{v2} = \frac{v_b(Q_2)}{v_{in}}$

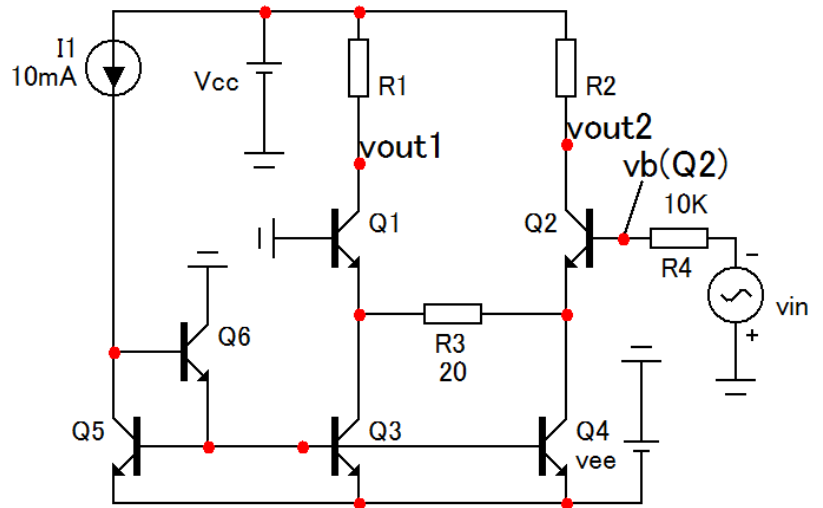

Answer:

a. $A_{v1} = \frac{v_{out}}{v_b(Q_2)} = \left(\frac{\beta}{1+\beta} \right) \frac{R_1}{2r_e + R_3} = 2.64$

b. $A_{v2} = \frac{R_{ib2}}{R_{ib2} + R_4} = \frac{(1+\beta)(2r_e + R_3)}{(1+\beta)(2r_e + R_3) + R_4} = 0.131$


10. All betas are infinity

- a. Calculate the DC voltage at the base of Q1 and Q2
 b. Calculate the DC voltage at the collector of Q1 and Q2
 c. Draw the small equivalent diagram
 d. Use the equivalent diagram to find the differential gain if the difference of the collector voltages is defined as the output voltage.

$$A_v = \frac{v_{c1} - v_{c2}}{v_i}$$

Answers:

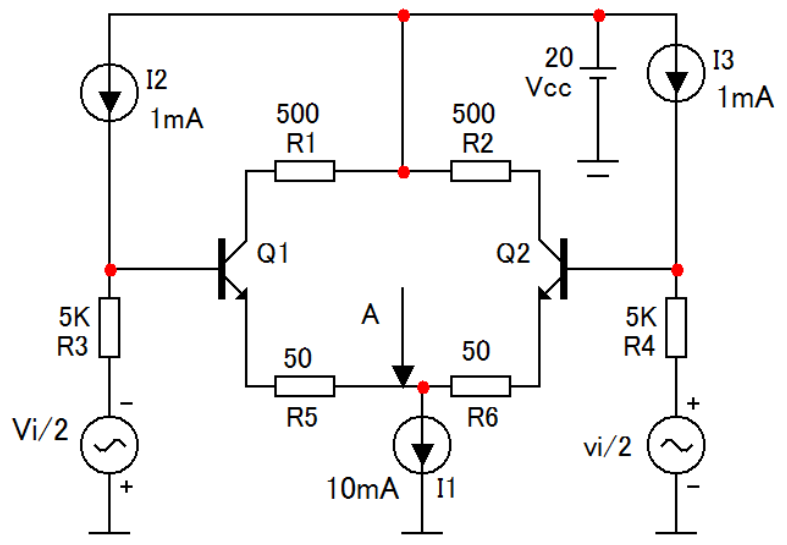
- a. $V_{b1}=5$ Volt
 b. $V_{c1}=17.5$ Volt
 c....
 d. $A_v=9.06$



11. ...

- a.
 b.

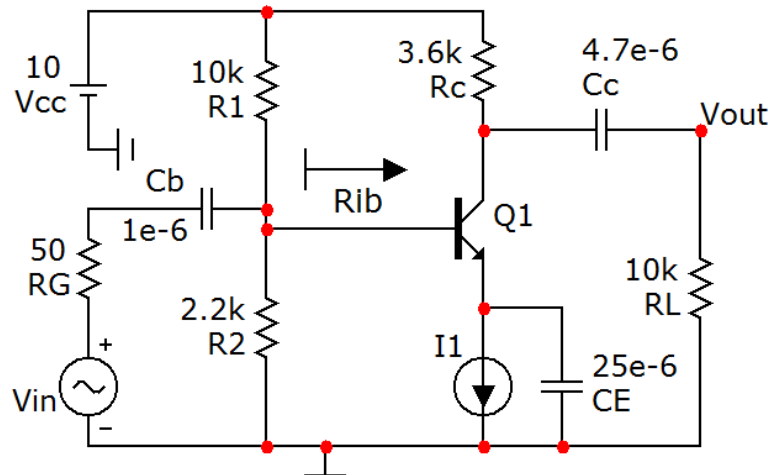1. $\beta_{Q1} = 20, I_1 = 1 \text{ mA}$
 $V_{in} = 0.001 \times \sin(2000\pi t)$
 I_1 is current source !




- a. Draw the small signal equivalent circuit, including the capacitors. Only equivalent T-model is allowed.
- b. Find the expression for calculating R_{ib} (assume that the emitter is grounded)
- c. Calculate the low-cutoff frequency [Hz] for $C_b = 1\mu\text{F}$ with $R_{ib} = 1000 \Omega$
- d. Calculate the low-cutoff frequency caused by C_c . ($C_c = 4.7\mu\text{F}$)
- e. Calculate the low-cutoff frequency for $C_e = 25\mu\text{F}$. Use $\beta = \infty$

Answers: a. Check sheets b. $R_{ib} = (1 + \beta)r_e$ c. $f_{-3dB} = 230\text{Hz}$ d. $f_{-3dB} = 2.49\text{Hz}$ e. $f_{-3dB} = 1538\text{Hz}$

2. $\beta_{Q1} = \beta_{Q2} = \infty$ & $V_{cc} = 15\text{V}$

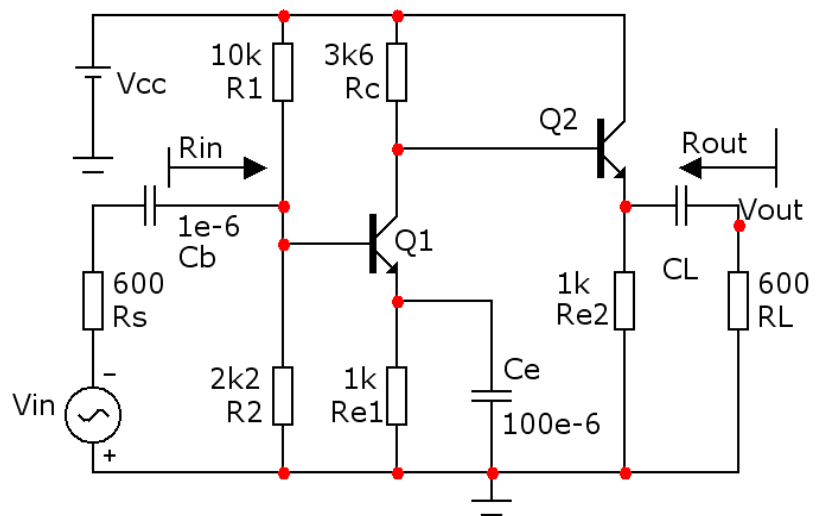- a. Calculate the collector currents of Q1 and Q2
Bereken de collectorstromen van Q1 en Q2



- b. Draw the small signal equivalent circuit, with short circuited capacitors.
Teken het kleinsignaal vervangingschema met kort gesloten condensatoren.
- c. Write down the expression to calculate the mid band gain. Gain definition is:

$$A_v = \frac{V_{out}}{V_{in}}$$



The numerical value is not requested.

Vermeld de uitdrukking waarmee de mid band versterking berekend kan worden. De versterking is gedefinieerd

als: $A_v = \frac{V_{out}}{V_{in}}$ Numerieke waarde wordt niet gevraagd.

- 3.
- a.
- b.
- c.

1. Given circuit and related graph

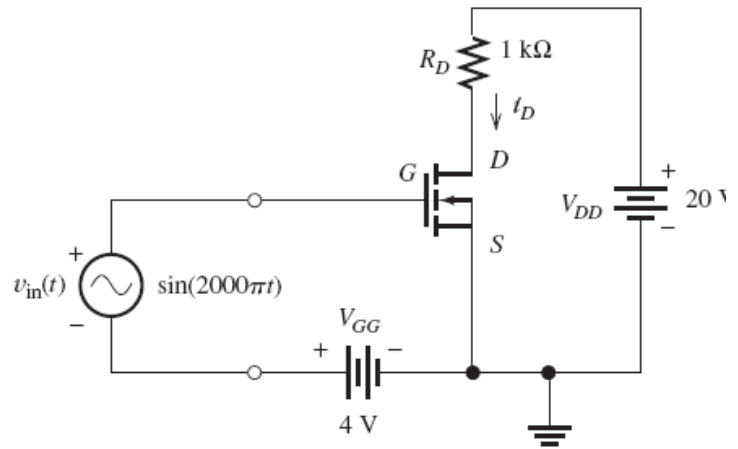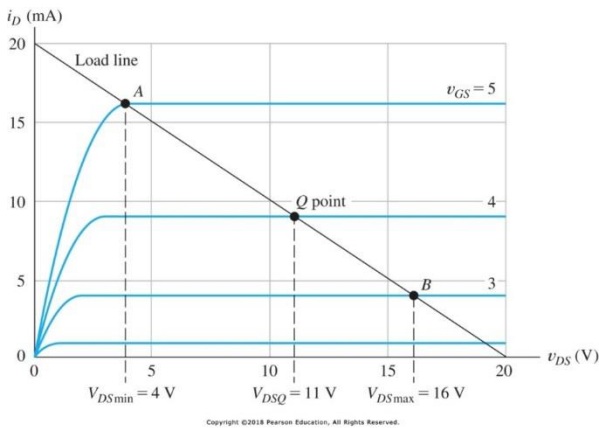


- Suppose the Qpoint is valid, what will be the not distorted maximum amplitude of the output signal? (voltage between drain and source)
- Suppose the Qpoint B is valid what will be the not distorted maximum amplitude of the output signal?
- Suppose the Qpoint A is valid what will be the not distorted maximum amplitude of the output signal?

Answers: a. 7 Volt top
 b. 4 Volt top
 c. 0 Volt

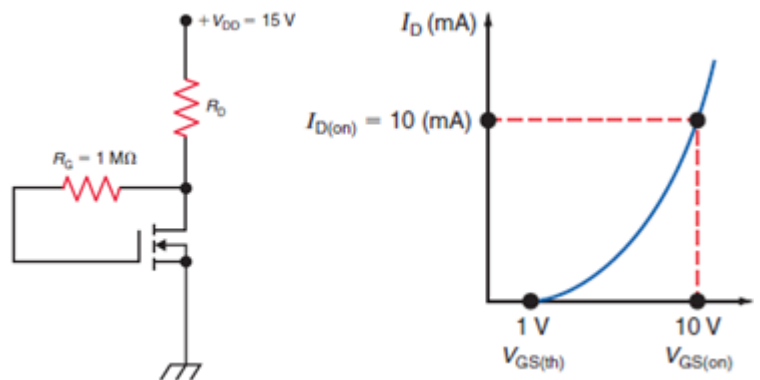2. See schematic and MOSFET characteristics

- Calculate R_D to make $I_D=10\text{mA}$
 Answer: 500Ω



3. $I_D = k(V_{GS} - V_{to})^2$

$$g_m = \frac{dI_d}{dV_{GS}} \approx \frac{\Delta I_d}{\Delta V_{GS}} g_m = 2k(V_{GS} - V_{to})$$

$V_{th}=2$ Volt and $K=0.004$

$V_{dd}=10$ Volt

- a. Calculate the DC drain voltage referred to ground
- b. Calculate midband signal voltage gain


$$\left(\text{def.} \therefore A_v = \frac{v_{RL}}{V_s} = \frac{V_{out}}{V_s} \right)$$

Answers: a. $V_d = V_{dd} - I_d R_d = 10 - 0.001 \times 1000 = 9$ Volt

b. $g_m = 2 \times 0.004 \times (2.5 - 2) = 0.004$ mA/V

$i_d = g_m v_{gs}$ and $v_d = i_d \times (R_d // R_L)$

$$A_v = \frac{v_{out}}{v_s} = 2$$

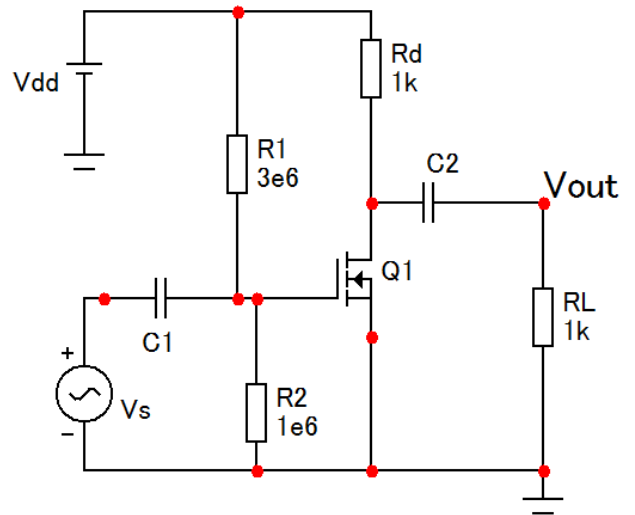

- 4. Given circuit to create a specific V_{GS} Voltage

Use: $I_d = K(V_{GS} - V_{to})^2$


$K = 200 \mu A / V^2$, $V_{to}=2$ Volt and $V_1=10$ Volt

- a. Calculate R to make $I_D=100 \mu A$
- b. Calculate V_{GS}

Answers: a. $R=72928 \Omega$

b. $V_{GS}=2.70$ Volt


- 5.
- 6.

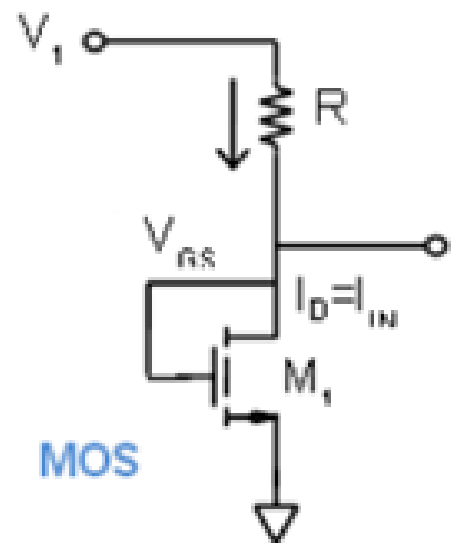

7.

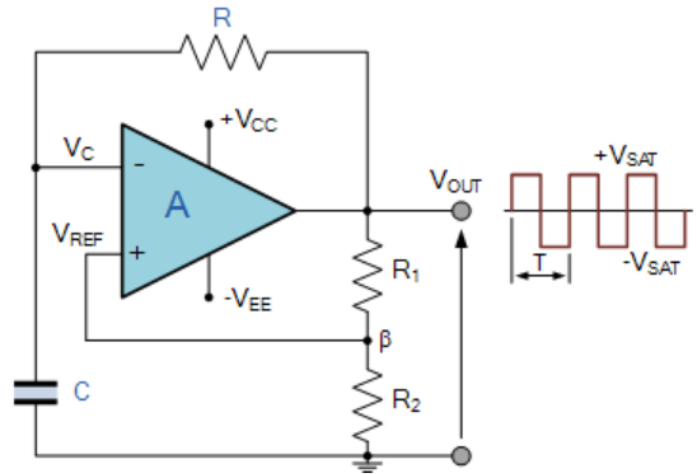1. The Opamp is ideal. $V_{cc}=10$ Volt, $V_{ee}= -5$ Volt
 $R_1=R_2=1K$, $R=1K$ and $C=1\mu F$

- Calculate the threshold voltages
 V_{UT} & V_{LT} ($V_{sat} = V_{cc}$)
- Find the expression for charging and discharging C
- Calculate the charging time and discharging time.
- Sketch the wave form $v_{cap}(t)$



Answers:

$$V_{UT} = \frac{R_2}{R_2 + R_1} V_{cc} = 5 \text{ Volt}, V_{LT} = \frac{R_2}{R_2 + R_1} V_{ee} = -2.5 \text{ Volt}$$

$$v_c(t) = V_{cc} - (V_{cc} - V_{LT}) e^{-\frac{t}{\tau_{ch}}}$$

$$v_c(t) = V_{ee} - (V_{ee} - V_{UT}) e^{-\frac{t}{\tau_{dis}}}$$

$$t_{ch} = \tau \ln \left(\frac{V_{LT} - V_{cc}}{V_{UT} - V_{cc}} \right) = (1e-3) \ln \left(\frac{-2.5 - 10}{5 - 10} \right) = 0.92 \text{ ms}$$

$$t_{dis} = \tau \ln \left(\frac{V_{UT} - V_{ee}}{V_{LT} - V_{ee}} \right) = (1e-3) \ln \left(\frac{5 - (-5)}{-2.5 - (-5)} \right) = 1.39 \text{ ms}$$


2. $R_1=R_4=1K$, $V_{cc}=-V_{ee}=10$ Volt and Opamp is ideal.
 $V_{out(max)}=V_{cc}$ and $V_{out(min)}=V_{ee}$
- Calculate R_2 and R_3 to create upper and lower threshold voltages of 6 Volt and -4 Volt
 - Calculate C_1 to make $\tau=1\text{ms}$

Answers:

$$a. V_{UT} = \frac{R_1}{R_1 + R_2} V_{cc} \quad R_2 = \frac{R_1(V_{cc} - V_{UT})}{V_{UT}}$$


$$V_{LT} = \frac{R_1}{R_1 + R_3} V_{ee} \quad R_3 = \frac{R_1(V_{ee} - V_{LT})}{V_{LT}}$$

$$b. C_1 = \frac{\tau}{R_4} = 1 \mu F$$

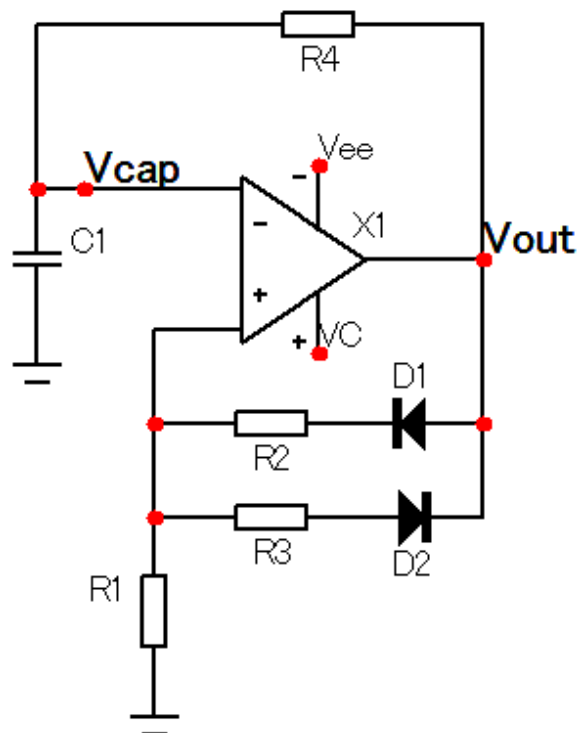

3. Frequency of oscillation is $f_r = \frac{1}{2\pi RC}$

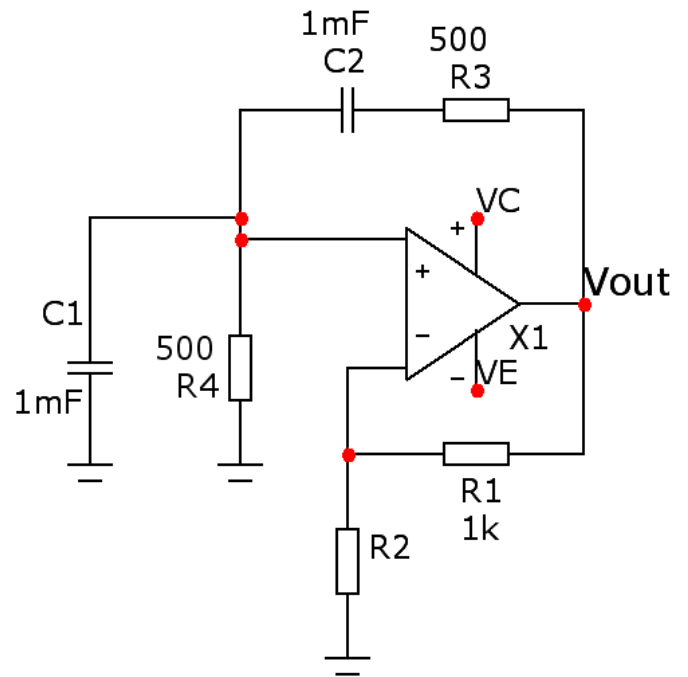- a. Calculate the frequency of oscillation
- b. What is the relationship between the voltage at the none inverting input and the output, in case the circuit oscillates.
- c. Calculate the critical value for R2
- d. Which component must be replaced by a bulb for gain control. The resistance of a bulb increase if the applied voltage increase (pos. temp. coefficient)



4. Phase locked loop

- a. Draw the blockdiagram of the PLL.
- b. What is the main function of the PLL ?
- c. Give a short description about the capture range (Lock range is not equal to the Cap. Range)
- d. Which block is responsible for the "lock speed"?

5.
 - a.
 - b.