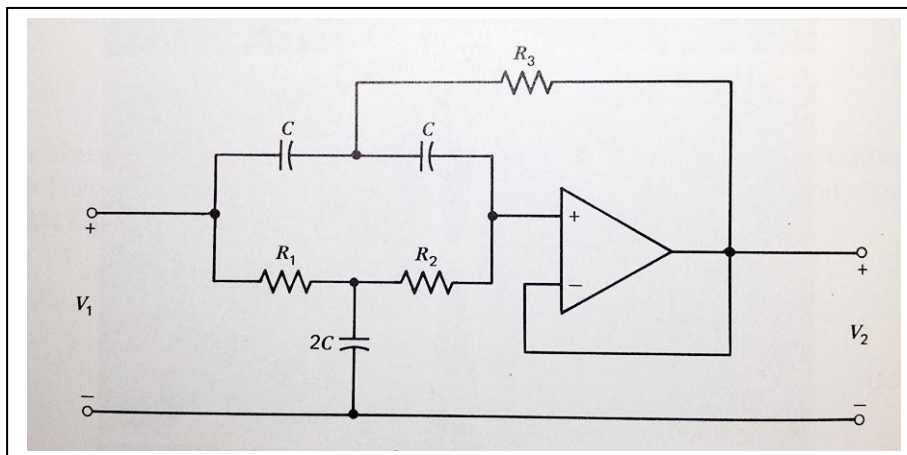


Assignment - 2



$$R_{1,2,3} = \dots\dots\Omega \quad C = \dots\dots\mu F$$

- 1 - Given the circuit, find its transfer function $H(s)$ in s-domain or $j\omega$ -domain in a symbolic expression.
- 2 - What is the order and DC gain of this filter circuit?
- 3 - Find the symbolic expression of the input impedance Z_{in} in s-domain.
- 4 - Verify your $H(s)$ and $Z_{in}(s)$ expression by doing a proper simulation of the circuit in LT-Spice with the given values. Investigate the influence of the value of C referring to $H(s)$.

- Deliver all results personally before end of the second examination week at the course responsible person.
- Only original work will be accepted.
- If there are questions about this assignment feel free to ask but do prepare good questions.
- More investigations in your circuit research will improve the chance for higher final marks.