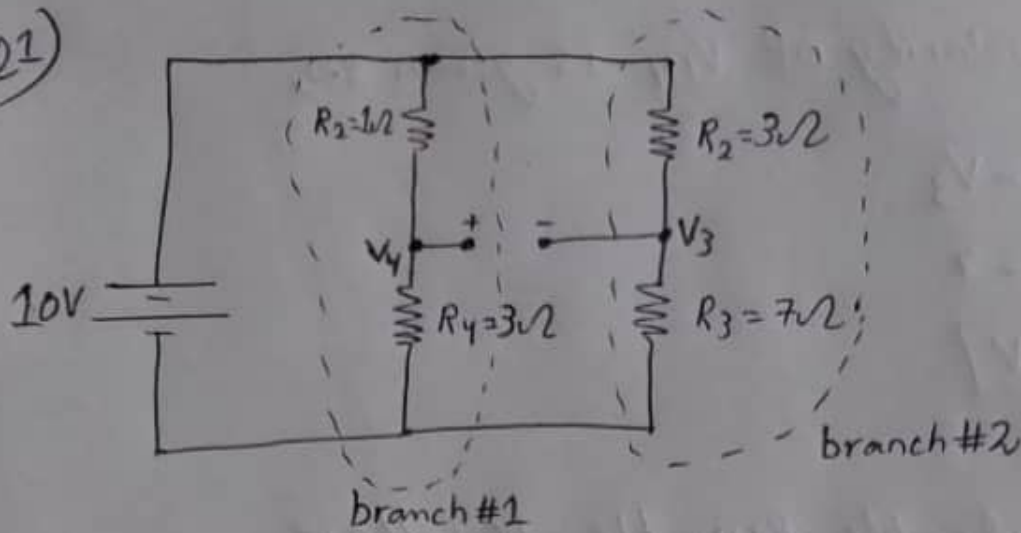


Q1)



Since branch #1 and branch #2 are parallel so applying voltage divider rule on  $R_4$  to calculate the voltage.

$$V_4 = \frac{V_{cc} R_4}{R_1 + R_4}$$

$$V_4 = \frac{(10)(3)}{1 + 3}$$

$$\boxed{V_4 = 7.5 \text{ V}}$$

applying voltage divider rule on  $R_3$  to calculate the voltage of  $R_3$ .

$$V_3 = \frac{V_{cc} R_3}{R_2 + R_3}$$

$$V_3 = \frac{(10)(7)}{3 + 7}$$

$$\boxed{V_3 = 7 \text{ V}}$$

since the polarity of  $V_{TH}$  is given so,


$$V_{TH} = V_4 - V_3$$

$$V_{TH} = 7.5 - 7$$

$$\boxed{V_{TH} = 0.5V}$$

For  $R_{TH}$ :-

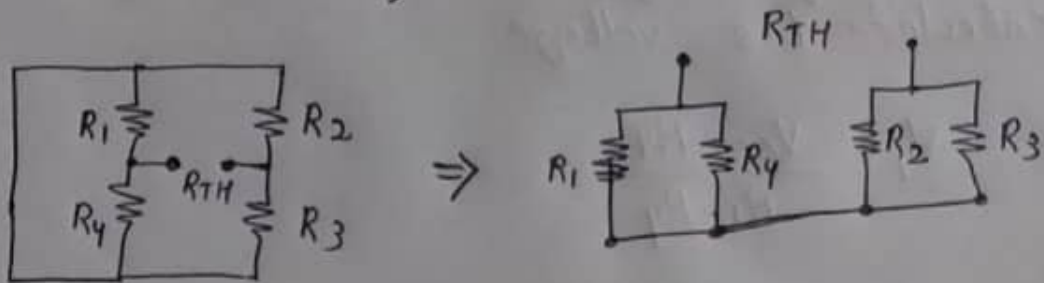when we calculate the  $R_{TH}$ , the DC voltage source will become short circuit so the circuit will be changed.




since  $R_1$  and  $R_4$  are parallel so,

$$R_5 = \frac{R_1 R_4}{R_1 + R_4} = \frac{(1)(3)}{(1) + (3)} = 0.75 \Omega$$

since  $R_2$  and  $R_3$  are parallel so,


$$R_6 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(3)(7)}{3 + 7} = 2.1 \Omega$$

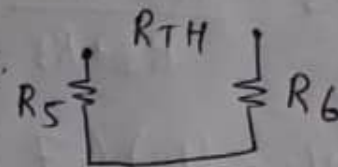$R_5$  and  $R_6$  will become in series.




$$R_{TH} = R_5 + R_6 = 0.75 + 2.1$$

$$\boxed{R_{TH} = 2.85 \Omega}$$

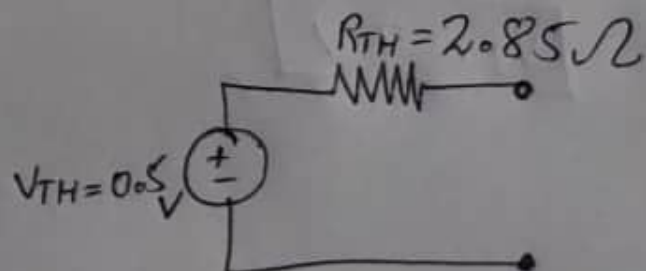

Q2)

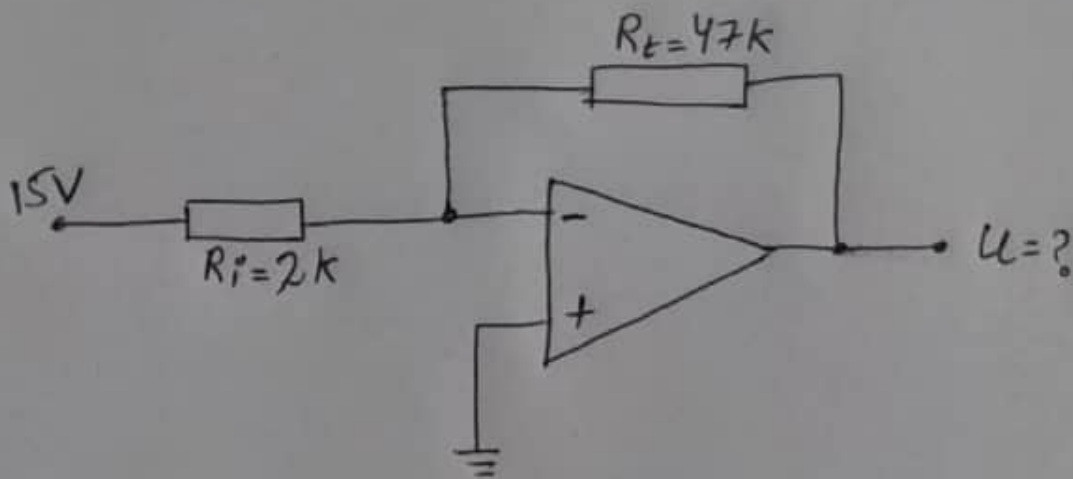

for Inverting Amplifier

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_t}{R_i}$$

$$V_{out} = -\frac{R_t}{R_i} \times V_{in}$$

$$V_{out} = -\frac{(47k)}{2k} \times (15)$$

$$U = V_{out} = -352.5 \text{ V} \quad \text{Ans}$$

For Amplitude:-

$$20 \log\left(\frac{R_t}{R_i}\right)$$

$$20 \log\left(\frac{47k}{2k}\right)$$

$$27.42 \text{ dB}$$